

MANAGEMENT AND ANALYSIS OF PHYSICS DATASET (MOD. A)

Fundamentals of Boolean Algebra
Combinatorial Functions

Postulates of the Boolean algebra





- Digital circuits or logic circuits deal with quantized signals (lack or presence of a signal)
- Fundamental elements of the digital computing
- “Logic” because we can apply analysis and synthesis methods derived from Boolean algebra
- Class of elements M and two operators \cdot and $+$

| | | | |
|-----|---------------------------|----------------------|--------------|
| P1: | $A + B = B + A$ | $AB = BA$ | Commutative |
| P2: | $A + 0 = A$ | $A \cdot 1 = A$ | Identity |
| P3: | $A + \bar{A} = 1$ | $A\bar{A} = 0$ | Complement |
| P4: | $A + BC = (A + B)(A + C)$ | $A(B + C) = AB + AC$ | Distributive |


- Duality of the operators

Postulates of the Boolean algebra

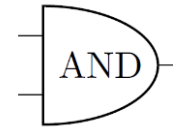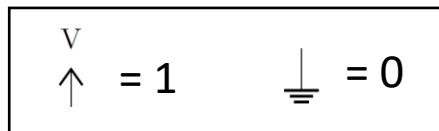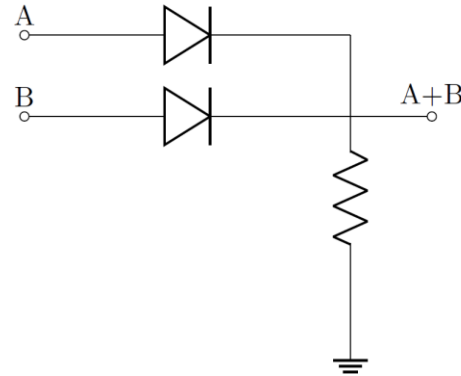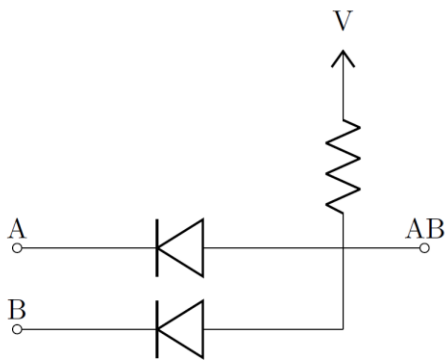- Proof of non contradiction: \cdot are connections, \cdot is the circuital operator AND and $+$ is the OR





| A | B | AB |
|---|---|----|
| 0 | 0 | 0 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

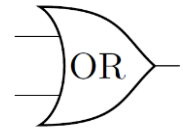


| A | B | A+B |
|---|---|-----|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 1 |

Postulates of the Boolean algebra

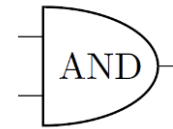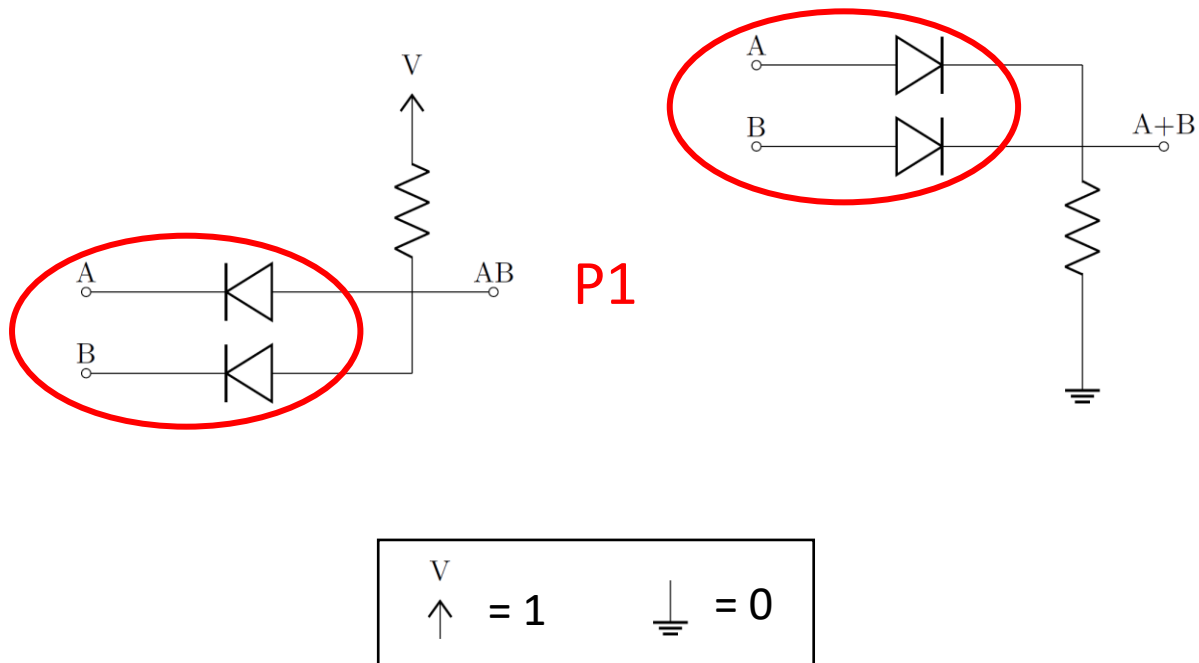- Proof of non contradiction: \cdot are connections, \cdot is the circuital operator AND and $+$ is the OR







| A | B | AB |
|---|---|----|
| 0 | 0 | 0 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

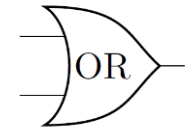


| A | B | A+B |
|---|---|-----|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 1 |

Postulates of the Boolean algebra

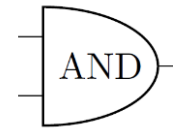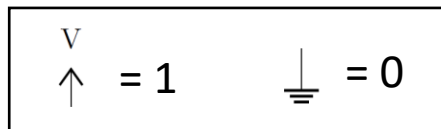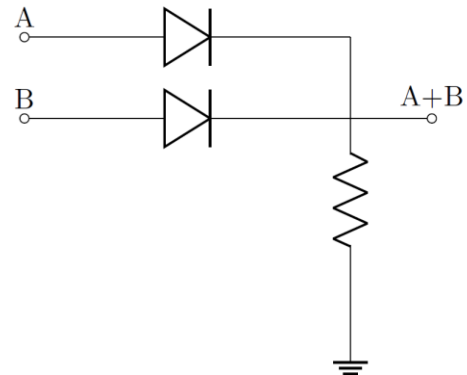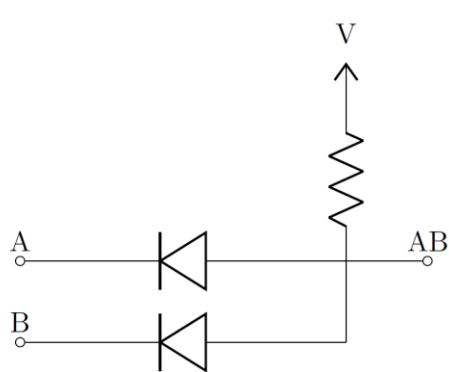- Proof of non contradiction: \cdot are connections, \cdot is the circuital operator AND and $+$ is the OR



| A | B | AB |
|---|---|----|
| 0 | 0 | 0 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

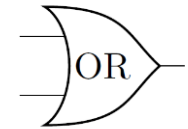


| A | B | A+B |
|---|---|-----|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 1 |

P2

Postulates of the Boolean algebra

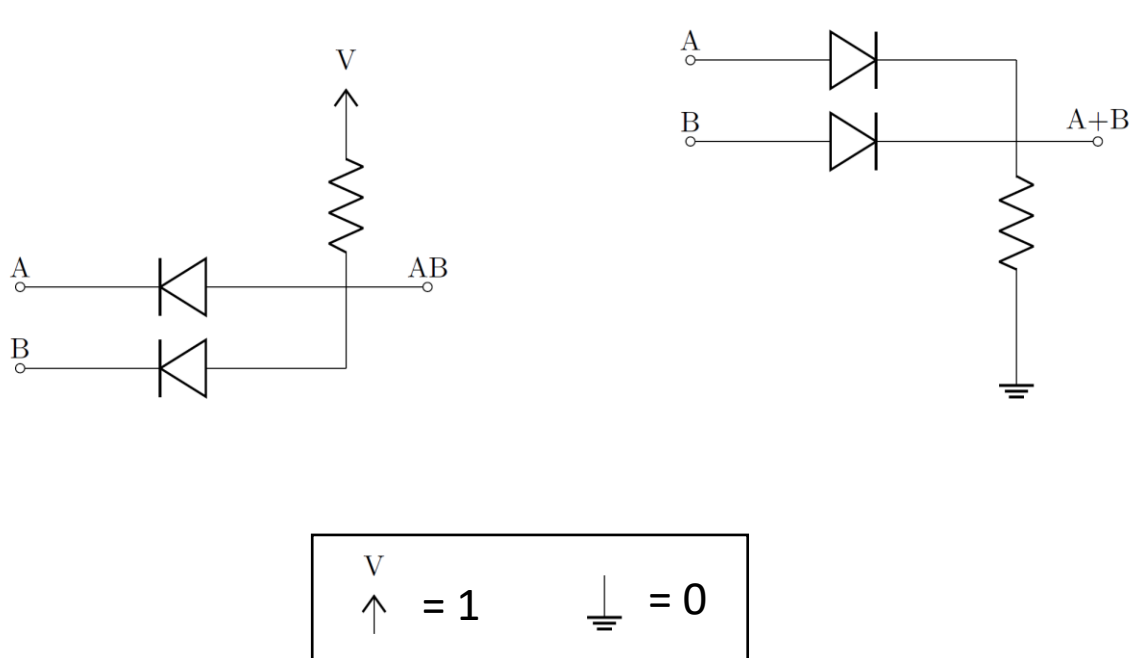- Proof of non contradiction: M are connections, \cdot is the circuital operator AND and $+$ is the OR



| AND | | | OR | | |
|-----|---|----|----|---|-----|
| A | B | AB | A | B | A+B |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 |


P3

Postulates of the Boolean algebra


- Proof of non contradiction: \cdot are connections, \cdot is the circuital operator AND and $+$ is the OR

P4

| A | B | C | A+BC | (A+B)(A+C) |
|---|---|---|------|------------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

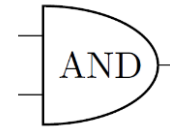



| A | B | AB |
|---|---|----|
| 0 | 0 | 0 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

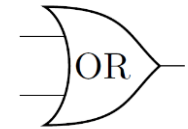

| A | B | A+B |
|---|---|-----|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 1 |

Postulates of the Boolean algebra

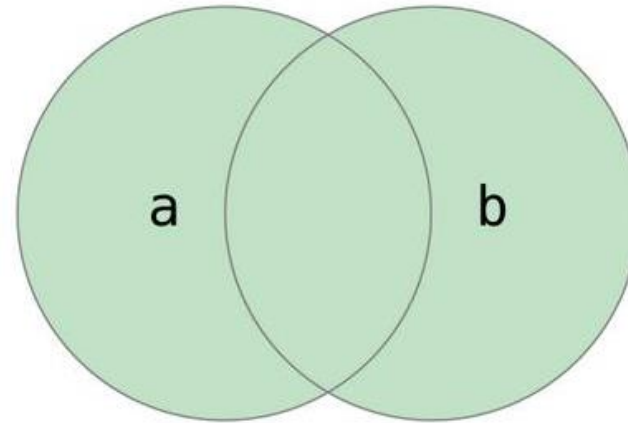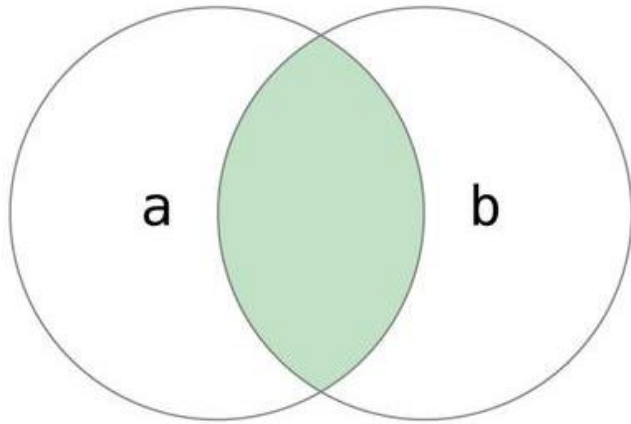- The postulates are valid also for other classes
- For instance: M is the class of all subsets of the set M , \cdot is the intersection and $+$ is the union
- Graphical representation can be used to quickly proof theorems



Simple theorems

T1: $A + A = A$

$$AA = A$$

Proof: $A + A = (A + A) \cdot 1 = (A + A)(A + \bar{A}) = A + A\bar{A} = A + 0 = A$

T2: $A + 1 = 1$

$$A \cdot 0 = 0$$

Proof: $A + 1 = (A + 1) \cdot 1 = (A + 1)(A + \bar{A}) = A + \bar{A} \cdot 1 = A + \bar{A} = 1$

T3: $A + AB = A$

$$A(A + B) = A$$

Proof: $A + AB = (A \cdot 1) + AB = A(1 + B) = A \cdot 1 = A$

De Morgan laws

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

Proof:

$$(A + B) + \overline{A} \cdot \overline{B} = (A + B + \overline{A})(A + B + \overline{B}) = (B + 1)(A + 1) = 1 \cdot 1 = 1$$

$$(A + B) \cdot \overline{A} \cdot \overline{B} = A \cdot \overline{A} \cdot \overline{B} + B \cdot \overline{A} \cdot \overline{B} = \overline{B} \cdot 0 + \overline{A} \cdot 0 = 0 + 0 = 0$$

From P3 we can conclude that $A+B$ is the complementary of $\overline{A} \cdot \overline{B}$

Generalization: the complementary of a Boolean function results from the exchange of the dual operators and from the exchange of the operands with their complement

Exercises

1. Demonstrate that $(A + B)(\overline{A} + C) = \overline{A}B + AC$
2. Demonstrate that $f(A, B) = \overline{A} \overline{B} + AB = \overline{f}(\overline{A}, B)$

Combinatorial functions

Combinatorial functions

- A simple way of describing a Boolean function is the truth table

| A | B | $f(A, B) = \overline{A} + \overline{B}$ |
|---|---|---|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

- It describes f as function of its input -> combinatory function
- Many functions can be built from the same truth table

$$\begin{aligned} f(A, B) &= \overline{A \cdot B} \\ &= \overline{A} \overline{B} + \overline{A} B + A \overline{B} \\ &= \overline{B} + \overline{A} B \end{aligned}$$

Which is the best?

Canonical form

- Minterm (m) of n variables is the Boolean product of all the variables where they appears only once (either in the complemented or uncomplemented form)
- They are 2^n . For instance, for $n = 2$ they are $\bar{A} \bar{B}$, $A \bar{B}$, $\bar{A} B$ and $A B$
- Similarly, Maxterm (M) can be defined for the sum

| A | B | Minterm | Maxterm |
|---|---|-------------------------|---------------------------|
| 0 | 0 | $m_0 = \bar{A} \bar{B}$ | $M_0 = \bar{A} + \bar{B}$ |
| 1 | 0 | $m_1 = A \bar{B}$ | $M_1 = A + \bar{B}$ |
| 0 | 1 | $m_2 = \bar{A} B$ | $M_2 = \bar{A} + B$ |
| 1 | 1 | $m_3 = A B$ | $M_3 = A + B$ |

Canonical form

- m_i is always equal to 0 except in one case (variables in line i)
- M_i is always equal to 1 except in one case (variables in line $2^n - 1 - i$)
- The product of two distinct minterms is always 0 and the sum of two distinct maxterm is always 1

$$\overline{m_i} = M_{2^n-1-i}$$

$$\overline{M_i} = m_{2^n-1-i}$$

$$\sum_{i=0}^{2^n-1} m_i = 1$$

$$\prod_{i=0}^{2^n-1} M_i = 0$$

Canonical form

- Combinatorial functions expressed as a sum of minterms or product of maxterms are said to be in canonical form

| A | B | $f(A, B) = \overline{A} + \overline{B}$ |
|---|---|---|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

| A | B | F_k |
|---|---|-------|
| 0 | 0 | f_0 |
| 1 | 0 | f_1 |
| 0 | 1 | f_2 |
| 1 | 1 | f_3 |

$$f(A, B) = m_0 + m_1 + m_2$$

$$f(A, B) = M_0$$

$$F_k = \sum_{i=0}^{2^n-1} f_i m_i$$

$$F_k = \prod_{i=0}^{2^n-1} (f_i + M_{2^n-1-i})$$

Canonical form

- All the possible Boolean function of n variables are 2^{2^n}


| f_0 | f_1 | f_2 | f_3 | F_k |
|-------|-------|-------|-------|--------------------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | NOR |
| 0 | 1 | 0 | 0 | $A\overline{B}$ |
| 1 | 1 | 0 | 0 | \overline{B} |
| 0 | 0 | 1 | 0 | $\overline{A}B$ |
| 1 | 0 | 1 | 0 | \overline{A} |
| 0 | 1 | 1 | 0 | XOR |
| 1 | 1 | 1 | 0 | $NAND$ |
| 0 | 0 | 0 | 1 | AND |
| 1 | 0 | 0 | 1 | \overline{XOR} |
| 0 | 1 | 0 | 1 | A |
| 1 | 1 | 0 | 1 | $A + \overline{B}$ |
| 0 | 0 | 1 | 1 | B |
| 1 | 0 | 1 | 1 | $\overline{A} + B$ |
| 0 | 1 | 1 | 1 | OR |
| 1 | 1 | 1 | 1 | 1 |

From function to circuit

- Canonical form is the most generic, but it is not the simplest
- For building a circuit it is better to simplify
- Passive circuits cannot be used because they degrades the signal after few logic levels -> active components at least in the output stage
- The simplest amplifier is the common emitter transistor -> signal inversion -> NAND or NOR
- Any combinatorial Boolean function can be written with them
 - The complement of a variable is done wiring together the two inputs or applying a 1 for NAND and 0 for NOR
 - By De Morgan NAND is the OR of complements and NOR is the AND of complements


From function to circuit

$$f = A B + \bar{A} \bar{B}$$

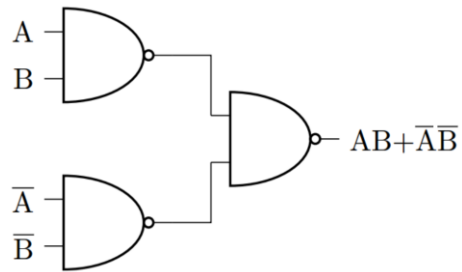


Sum of products

$$f = (A + \bar{B})(\bar{A} + B)$$

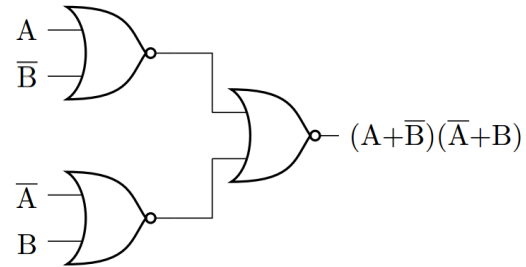


Product of sums

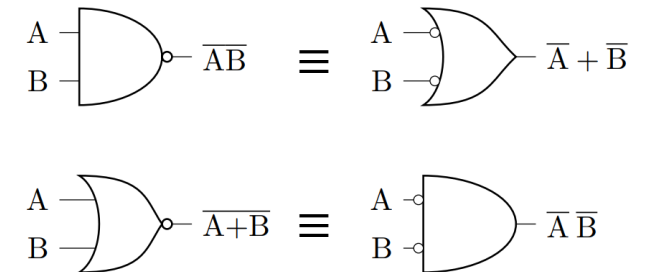

De Morgan duality

XOR

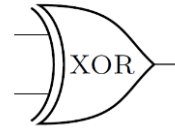- $A \oplus B = \bar{A} \oplus \bar{B} = A \bar{B} + \bar{A} B$
- $\overline{A \oplus B} = \bar{A} \oplus B = \bar{A} \bar{B} + A B$



- $\bar{A} = 1 \oplus A$
- $A + B = \overline{\bar{A} \bar{B}} = 1 \oplus [(1 \oplus A)(1 \oplus B)]$
- $A B = \overline{\bar{A} + \bar{B}} = 1 \oplus [(1 \oplus A) + (1 \oplus B)]$

| A | B | $A \oplus B$ |
|---|---|--------------|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

| | | |
|---|-------|-------|
| | A | |
| B | m_3 | m_2 |
| | m_1 | m_0 |

| | | | | |
|---|-------------|-------|-------|-------|
| | -----A----- | | | |
| B | m_3 | m_7 | m_6 | m_2 |
| | m_1 | m_5 | m_4 | m_0 |
| | -----C----- | | | |

| | | | | |
|---|-------------|----------|----------|----------|
| | -----A----- | | | |
| B | m_3 | m_7 | m_6 | m_2 |
| | m_{11} | m_{15} | m_{14} | m_{10} |
| | m_9 | m_{13} | m_{12} | m_8 |
| | m_1 | m_5 | m_4 | m_0 |
| | -----C----- | | | |
| | | | | D |

Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

| | | |
|---|-------|-------|
| | A | |
| B | m_3 | m_2 |
| | m_1 | m_0 |

$$m_0 = \overline{A}\overline{B}$$

| | | | | |
|---|-------|-------|-------|-------|
| | A | | | |
| B | m_3 | m_7 | m_6 | m_2 |
| | m_1 | m_5 | m_4 | m_0 |

| | | | | |
|---|----------|----------|----------|----------|
| | A | | | |
| B | m_3 | m_7 | m_6 | m_2 |
| | m_{11} | m_{15} | m_{14} | m_{10} |
| | m_9 | m_{13} | m_{12} | m_8 |
| | m_1 | m_5 | m_4 | m_0 |
| C | | | | D |

Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

| | | |
|---|-------|-------|
| A | | |
| B | m_3 | m_2 |
| | m_1 | m_0 |

$$m_1 = A\bar{B}$$

| | | | | |
|-------------|-------|-------|-------|-------|
| -----A----- | | | | |
| B | m_3 | m_7 | m_6 | m_2 |
| | m_1 | m_5 | m_4 | m_0 |
| -----C----- | | | | |

| | | | | |
|-------------|----------|----------|----------|----------|
| -----A----- | | | | |
| -----B----- | m_3 | m_7 | m_6 | m_2 |
| | m_{11} | m_{15} | m_{14} | m_{10} |
| | m_9 | m_{13} | m_{12} | m_8 |
| | m_1 | m_5 | m_4 | m_0 |
| -----C----- | | | | |
| -----D----- | | | | |

Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

| | | |
|---|-------|-------|
| | A | |
| B | m_3 | m_2 |
| | m_1 | m_0 |

$$m_2 = \bar{A}B$$

| | | | | |
|---|-------------|-------|-------|-------|
| | -----A----- | | | |
| B | m_3 | m_7 | m_6 | m_2 |
| | m_1 | m_5 | m_4 | m_0 |
| | -----C----- | | | |

| | | | | |
|-------------|-------------|----------|----------|-------------|
| | -----A----- | | | |
| -----B----- | m_3 | m_7 | m_6 | m_2 |
| | m_{11} | m_{15} | m_{14} | m_{10} |
| | m_9 | m_{13} | m_{12} | m_8 |
| | m_1 | m_5 | m_4 | m_0 |
| | -----C----- | | | |
| | | | | -----D----- |

Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

| | |
|---|-------|
| A | |
| B | m_3 |
| | m_2 |
| | m_1 |
| | m_0 |

$$m_3 = AB$$

| | | | |
|---|-------|-------|-------|
| A | | | |
| B | m_3 | m_7 | m_6 |
| | m_2 | m_5 | m_4 |
| | m_1 | m_0 | |
| C | | | |

| | | | |
|---|----------|----------|----------|
| A | | | |
| B | m_3 | m_7 | m_6 |
| | m_{11} | m_{15} | m_{14} |
| | m_9 | m_{13} | m_{12} |
| | m_1 | m_5 | m_4 |
| | m_0 | | |
| C | | | |
| D | | | |

Graphical simplification

- $f = \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + \overline{A}B\overline{C}\overline{D} + AB\overline{C}\overline{D} + A\overline{B}C\overline{D} + AB\overline{C}\overline{D} + A\overline{B}CD + ABCD$

| | | | | |
|-------------|----------|----------|----------|-------------|
| -----A----- | | | | |
| -----B----- | m_3 | m_7 | m_6 | m_2 |
| | m_{11} | m_{15} | m_{14} | m_{10} |
| | m_9 | m_{13} | m_{12} | m_8 |
| | m_1 | m_5 | m_4 | m_0 |
| -----C----- | | | | -----D----- |

Graphical simplification

- $f = \overline{A} \overline{B} \overline{C} \overline{D} + A \overline{B} \overline{C} \overline{D} + \overline{A} B \overline{C} \overline{D} + A B \overline{C} \overline{D} + A \overline{B} C \overline{D} + A B C \overline{D} + A \overline{B} C D + A B C D$
- $f = AC + \overline{C} \overline{D} \rightarrow \text{NAND}$

| | | | |
|-------------|----------|----------|----------|
| -----A----- | | | |
| -----B----- | m_3 | m_7 | m_6 |
| | m_{11} | m_{15} | m_{14} |
| | m_9 | m_{13} | m_{12} |
| | m_1 | m_5 | m_4 |
| -----C----- | | | |
| -----D----- | | | |

Graphical simplification

- $f = \overline{A} \overline{B} \overline{C} \overline{D} + A \overline{B} \overline{C} \overline{D} + \overline{A} B \overline{C} \overline{D} + A B \overline{C} \overline{D} + A \overline{B} C \overline{D} + A B C \overline{D} + A \overline{B} C D + A B C D$
- $f = A C + \overline{C} \overline{D} \rightarrow \text{NAND}$

A 4x4 Karnaugh map for the function f(A, B, C, D). The map is a 4x4 grid of cells, each labeled with a minterm m_i. The cells are shaded gray if they are part of the function f, and white otherwise. The shaded cells are m₃, m₇, m₁₅, m₁₃, m₅, m₁, m₀, and m₂. The unshaded cells are m₆, m₁₁, m₁₄, m₁₀, m₉, m₁₂, m₈, and m₄. The map is labeled with variables A, B, C, and D. A is at the top, B is on the left, C is at the bottom, and D is on the right. The map is a 4x4 grid of cells, each labeled with a minterm m_i. The cells are shaded gray if they are part of the function f, and white otherwise. The shaded cells are m₃, m₇, m₁₅, m₁₃, m₅, m₁, m₀, and m₂. The unshaded cells are m₆, m₁₁, m₁₄, m₁₀, m₉, m₁₂, m₈, and m₄. The map is labeled with variables A, B, C, and D. A is at the top, B is on the left, C is at the bottom, and D is on the right.

| | | | | | |
|-------------|-----------------|-----------------|-----------------|-----------------|-------------|
| | -----A----- | | | | |
| -----B----- | m ₃ | m ₇ | m ₆ | m ₂ | -----D----- |
| | m ₁₁ | m ₁₅ | m ₁₄ | m ₁₀ | |
| | m ₉ | m ₁₃ | m ₁₂ | m ₈ | |
| | m ₁ | m ₅ | m ₄ | m ₀ | |
| | -----C----- | | | | |

Graphical simplification

- $f = \overline{A} \overline{B} \overline{C} \overline{D} + A \overline{B} \overline{C} \overline{D} + \overline{A} B \overline{C} \overline{D} + A B \overline{C} \overline{D} + A \overline{B} C \overline{D} + A B C \overline{D} + A \overline{B} C D + A B C D$
- $f = A C + \overline{C} \overline{D} \rightarrow \text{NAND}$
- $\overline{f} = \overline{A} C + \overline{C} D$
- $f = (A + \overline{C})(C + \overline{D}) \rightarrow \text{NOR}$

| | | | | |
|-------------|----------|----------|-------------|----------|
| -----A----- | | | | |
| -----B----- | m_3 | m_7 | m_6 | m_2 |
| | m_{11} | m_{15} | m_{14} | m_{10} |
| | m_9 | m_{13} | m_{12} | m_8 |
| | m_1 | m_5 | m_4 | m_0 |
| -----C----- | | | | |
| | | | -----D----- | |

Exercises

1. Demonstrate that $(A \oplus B) \oplus C = A \oplus (B \oplus C) = B \oplus (A \oplus C)$
2. Simplify $AB\bar{C} + ABC + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C + \bar{A}\bar{B}C$

Examples of combinatorial logic

Adder

- Elementary cell for adding two bits (binary digit)
- Extension to two n-bits numbers

| A_i | B_i | C_i | S_i | C_{i+1} |
|-------|-------|-------|-------|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

$$S_i = (A \bar{B} \bar{C} + \bar{A} B \bar{C} + \bar{A} \bar{B} C + A B C)_i$$


$$C_{i+1} = (A B \bar{C} + A \bar{B} C + \bar{A} B C + A B C)_i$$

$$S_i = (A \bar{B} + \bar{A} B)_i \bar{C}_i + (\bar{A} \bar{B} + A B)_i C_i = (A \oplus B)_i \oplus C_i$$

$$C_{i+1} = (A B + A C + B C)_i$$

Adder

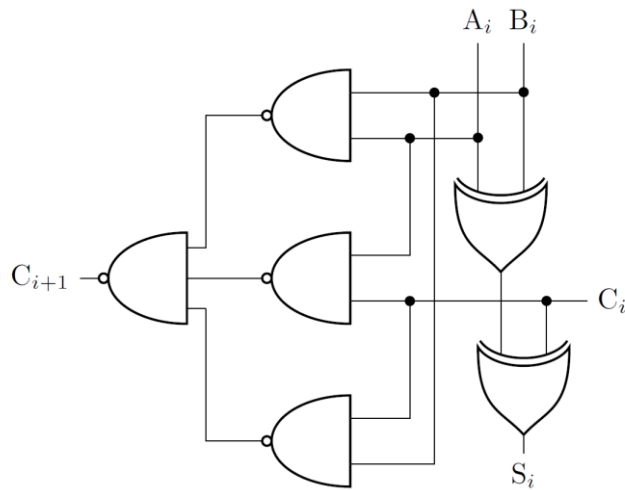- Elementary cell for adding two bits (binary digit)
- Extension to two n-bits numbers



$$S_i = (A \bar{B} \bar{C} + \bar{A} B \bar{C} + \bar{A} \bar{B} C + A B C)_i$$



$$C_{i+1} = (A B \bar{C} + A \bar{B} C + \bar{A} B C + A B C)_i$$

$$S_i = (A \bar{B} + \bar{A} B)_i \bar{C}_i + (\bar{A} \bar{B} + A B)_i C_i = (A \oplus B)_i \oplus C_i$$

$$C_{i+1} = (A B + A C + B C)_i$$

Adder

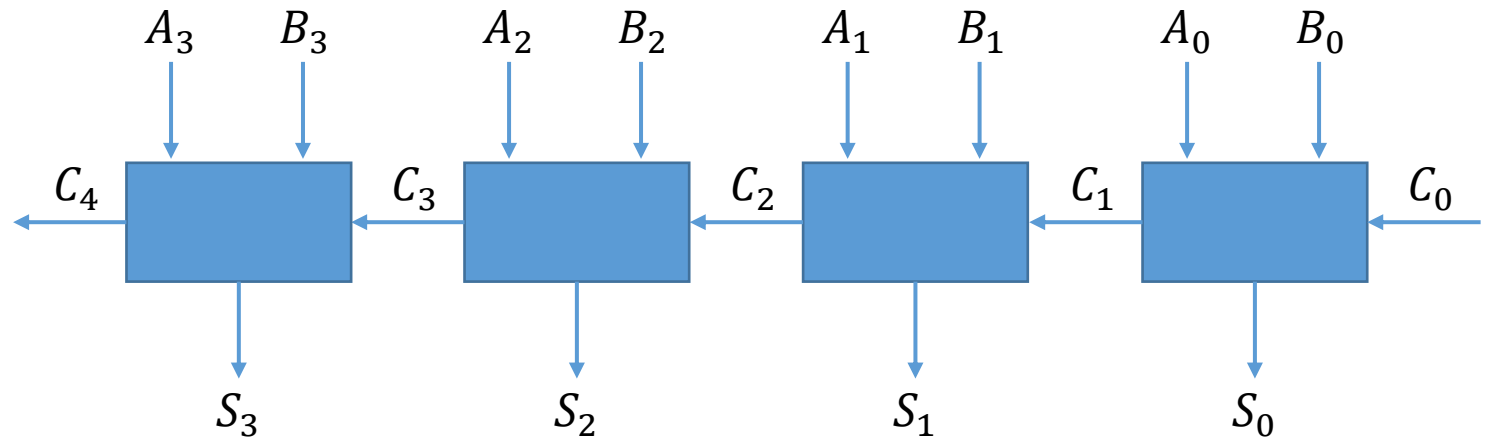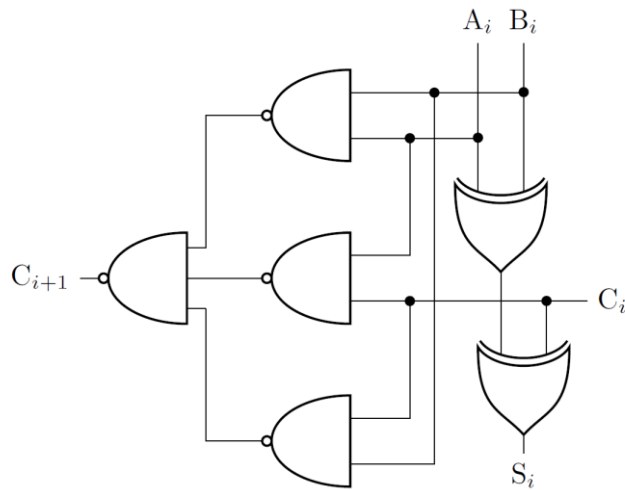- Elementary cell for adding two bits (binary digit)
- Extension to two n-bits numbers



Subtractor

- Exercise
 - Draw the circuit
 - Can be easily obtained from an adder?

Adder

- Modular adder has a propagation delay that depends on the number of bits (n)
- Carry propagation delay: $2T_P \cdot n$
- Carry can be calculated in parallel
- Carry-lookahead
 - Generate a carry if A and B are 1: $G_i = A_i B_i$
 - Propagate a carry if A or B are 1: $P_i = A_i + B_i$ but also if $P_i = A_i \oplus B_i$
- $C_{i+1} = G_i + C_i P_i$
- $C_4 = A_3 B_3 + A_2 B_2 (A_3 \oplus B_3) + A_1 B_1 (A_2 \oplus B_2) (A_3 \oplus B_3) + A_0 B_0 (A_1 \oplus B_1) (A_2 \oplus B_2) (A_3 \oplus B_3) + C_0 (A_0 \oplus B_0) (A_1 \oplus B_1) (A_2 \oplus B_2) (A_3 \oplus B_3)$
- Parallel carry propagation delay: $3T_P$

Parity generator

- The parity bit is a bit that added to the data makes the total number of ones (1s) even (even parity) or odd (odd parity)
- Parity is used for error detection during data transmission
- For instance, 1001010 has $P_{odd} = 0$ and $P_{even} = 1$
- Elementary cell for odd parity generation
- Extension to two n-bits numbers


| D_i | P_i | P_{i+1} |
|-------|-------|-----------|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

$$P_{i+1} = (D \bar{P} + \bar{D} P)_i = (D \oplus P)_i$$

$$P_0 = 1$$


Parity generator

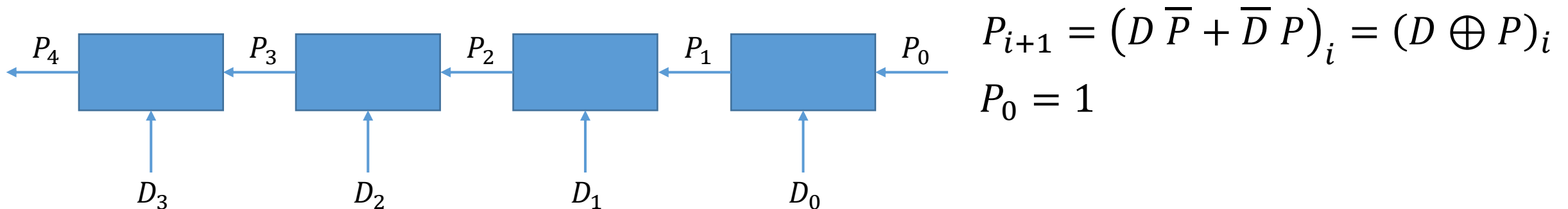- The parity bit is a bit that added to the data makes the total number of ones (1s) even (even parity) or odd (odd parity)
- Parity is used for error detection during data transmission
- For instance, 1001010 has $P_{odd} = 0$ and $P_{even} = 1$
- Elementary cell for odd parity generation
- Extension to two n-bits numbers



Parity generator

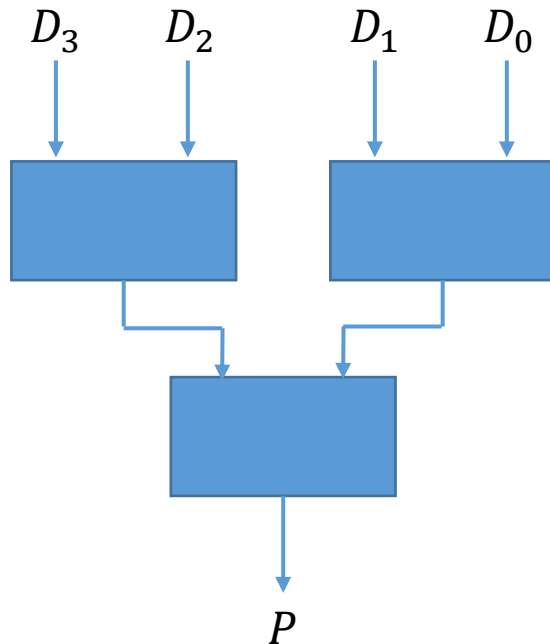- And for even parity generator?
 - Just change P_0
- As for the adder we can limit the propagation time with a module that works in parallel
- It is possible to connect the single module in a tree-like structure




$$P = (D_0 \oplus D_1) \oplus (D_2 \oplus D_3)$$

Comparison

- For comparing two binary numbers (a, b) , three output values are needed -> two output bits (N, M)
- Modular approach for n-bits extension

| | N | M |
|---------|-----|-----|
| $a > b$ | 0 | 1 |
| $a < b$ | 1 | 0 |
| $a = b$ | 0 | 0 |

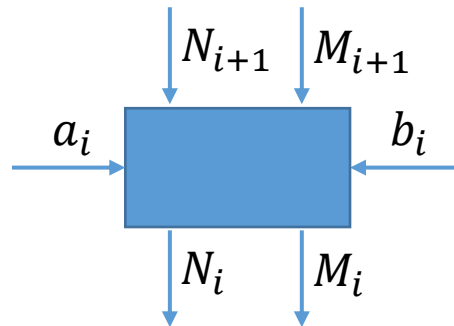


| a_i | b_i | N_{i+1} | M_{i+1} | N_i | M_i |
|-------|-------|-----------|-----------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | X | X |
| 1 | 0 | 1 | 1 | X | X |
| 0 | 1 | 1 | 1 | X | X |
| 1 | 1 | 1 | 1 | X | X |

Comparison

- For comparing two binary numbers (a, b) , three output values are needed \rightarrow two output bits (N, M)
- Modular approach for n-bits extension

| | N | M |
|---------|-----|-----|
| $a > b$ | 0 | 1 |
| $a < b$ | 1 | 0 |
| $a = b$ | 0 | 0 |

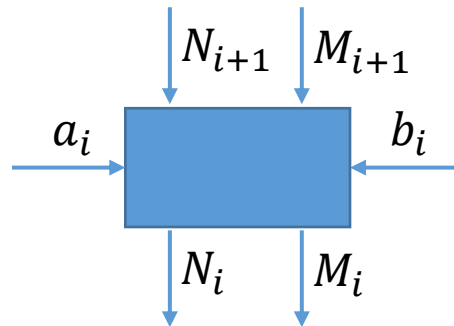

Redundant terms

| a_i | b_i | N_{i+1} | M_{i+1} | N_i | M_i |
|-------|-------|-----------|-----------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | X | X |
| 1 | 0 | 1 | 1 | X | X |
| 0 | 1 | 1 | 1 | X | X |
| 1 | 1 | 1 | 1 | X | X |

Comparison

- For comparing two binary numbers (a, b) , three output values are needed -> two output bits (N, M)
- Modular approach for n-bits extension

$$N_i = N_{i+1} + \overline{a_i} b_i \overline{M_{i+1}}$$


$$M_i = M_{i+1} + a_i \overline{b_i} \overline{N_{i+1}}$$

Redundant terms

| a_i | b_i | N_{i+1} | M_{i+1} | N_i | M_i |
|-------|-------|-----------|-----------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | X | X |
| 1 | 0 | 1 | 1 | X | X |
| 0 | 1 | 1 | 1 | X | X |
| 1 | 1 | 1 | 1 | X | X |


Multiplexer

- A Mux selects one signal among 2^n (D_i) thanks to n address lines (S_j)
- For $n = 1$, two levels of NAND ports can easily implement it
- Any combinatorial function can be generated connecting the address lines to the variables and connecting 1 to D_i if the minterm m_i is present, 0 otherwise
- A Demux applies the inverse operation
- It can be used as decoder because it selects the output line D_i corresponding to the minterm m_i

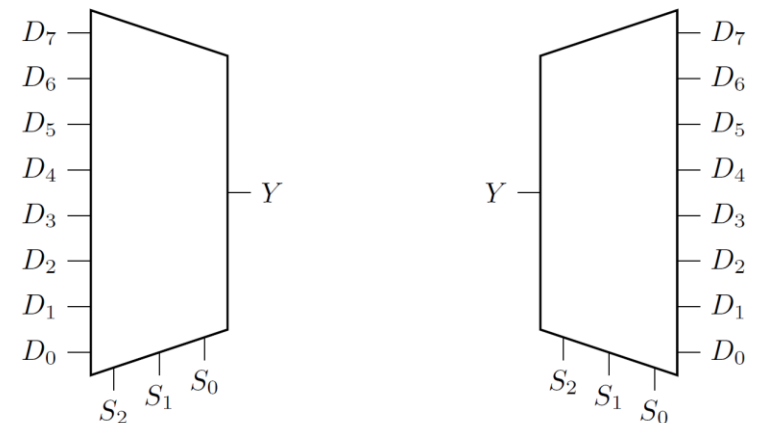


Tristate

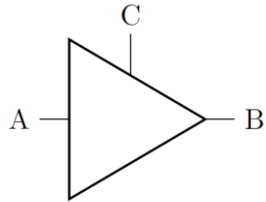- It is used for developing bidirectional connections
- Many data buses are usually tristate because they are used to link devices that can be both source and sink of information
- A control line is used for putting the output in high-impedance




| <i>A</i> | <i>C</i> | <i>B</i> |
|----------|----------|----------|
| 0 | 0 | Z |
| 1 | 0 | Z |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

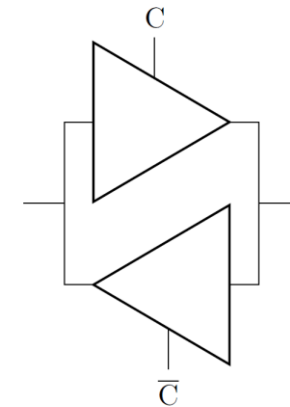



Programmable Logic Array

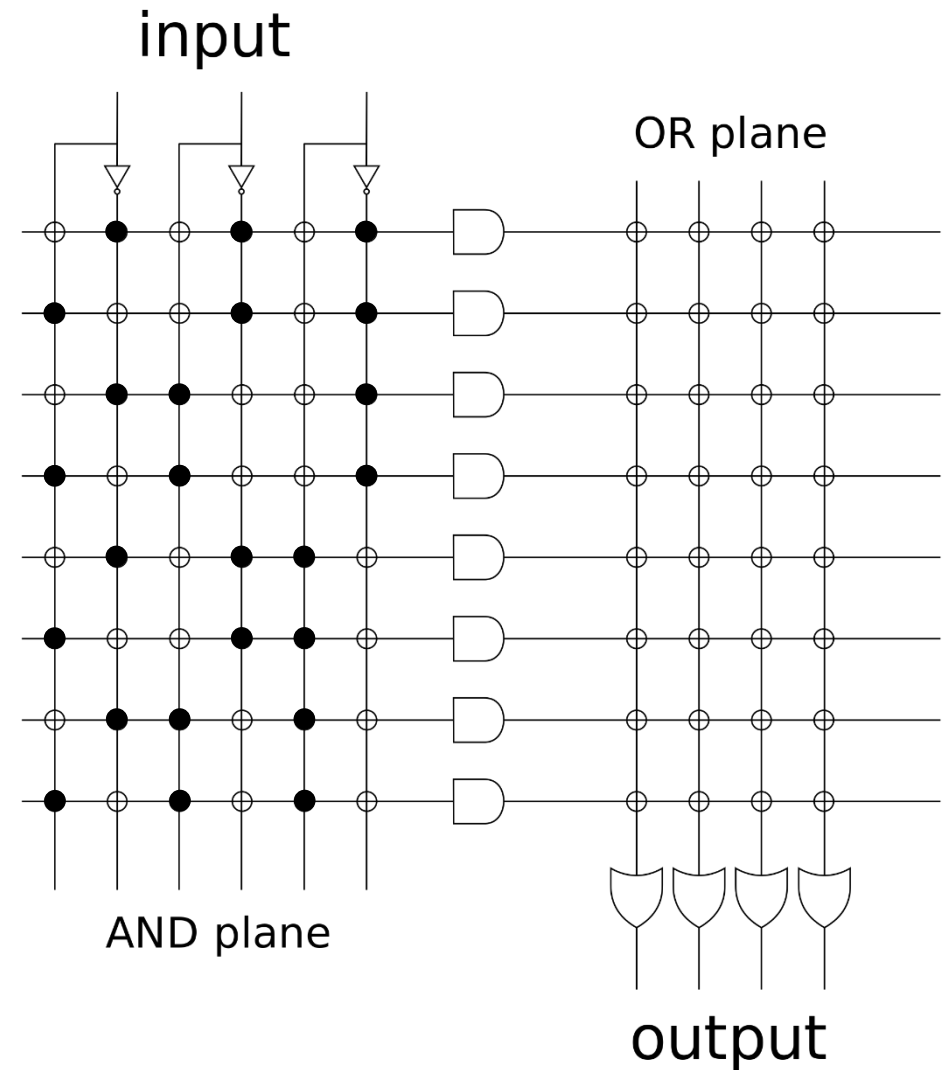- PLA consists of an AND array connected to an OR array
- Constant propagation delay
- It can build any sum of products
- The AND array can be fixed while the OR array is programmable
- Programmable logic-planes grow too quickly in size as the number of inputs is increased



Field-Programmable Gate Array

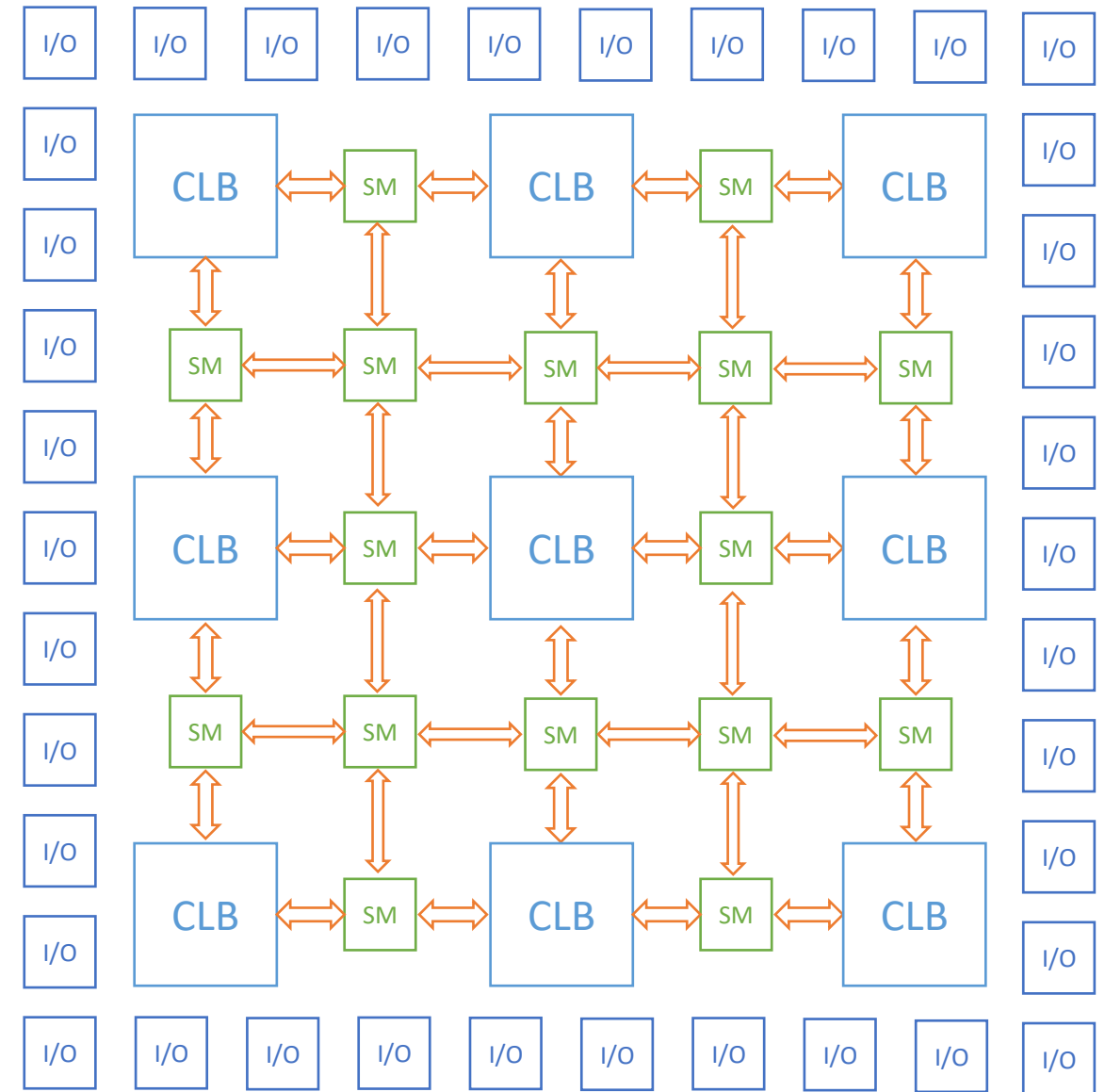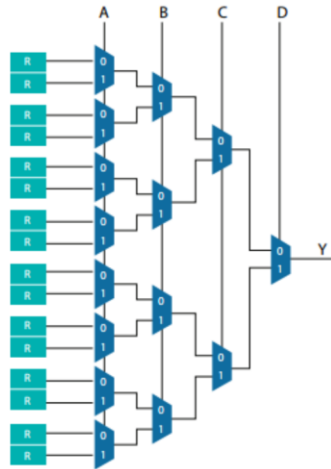- Programmable logic blocks linked by programmable interconnections
- Programmable Input and Output
- Configurable Logic Block can be either a combinatorial or a sequential circuit
- Look up tables are used to implement the truth table of a combinatorial function



Exercise

- Design a circuit able to compare two 2-bit numbers at a time